


CSN6114-COMPUTER ARCHITECTURE & ORG

T23L_G1

Name	Student ID
David Ting Zi Xiang	242UC244PE
KOO JUN WEI	243UC246DX
Chong Jia Yi	243UC246LW
Tay Yue	242UC244PN


1. Perform the study of the truth table of the following logic gates and verify the truth table of the gates experimentally.

2 input NAND gate

 

Two Input NAND gate		
A	B	$Y = \overline{A \cdot B}$
0	0	1
0	1	1
1	0	1
1	1	0


2 input NOR gate

 

TRUTH TABLE


INPUTS		OUTPUT
X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	0

3 input AND gate

 


Truth Table			
Input A	Input B	Input C	$Y = (A \cdot B \cdot C)$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

2 input XOR gate

 


A	B	Output
0	0	0
1	0	1
0	1	1
1	1	0

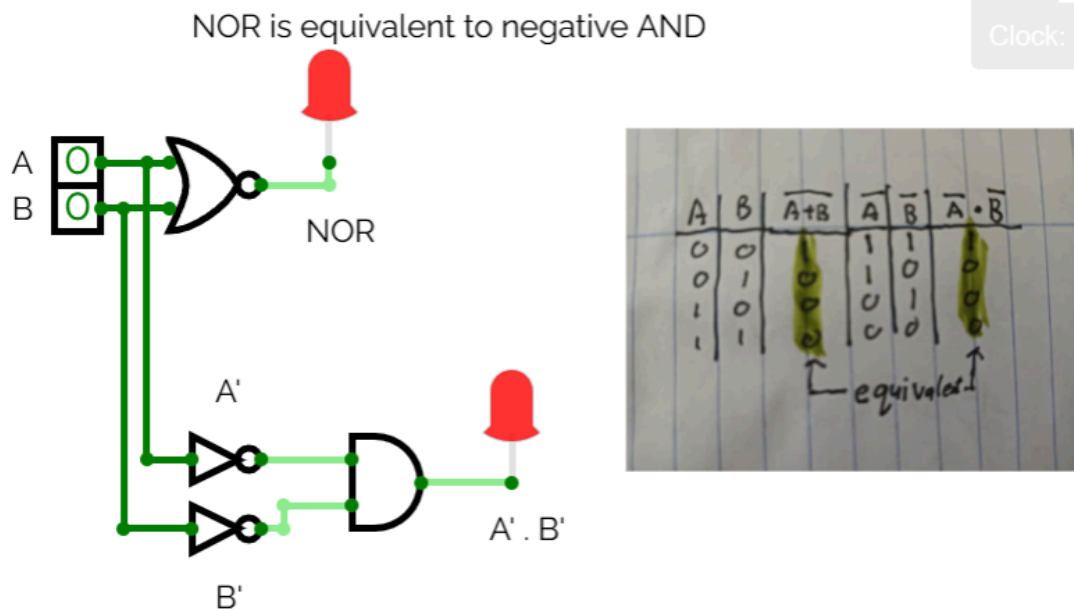2. (i) Prove that NOR gate is equivalent to a negative AND gate by constructing a simple circuit using NOT and AND gates and verify the truth table experimentally.



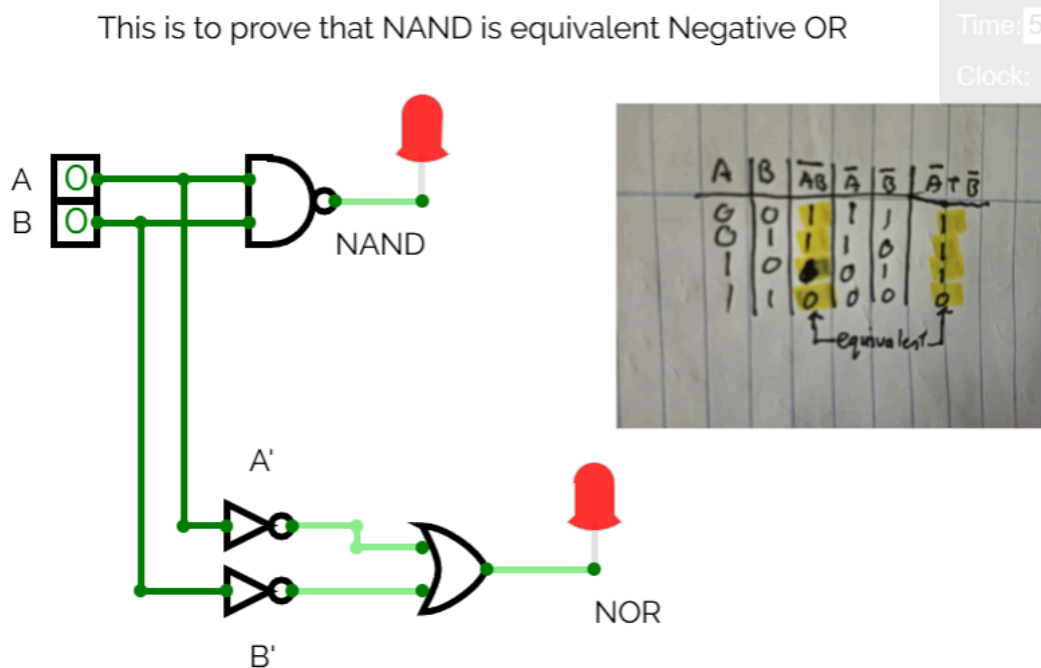(ii) Prove that NAND gate is equivalent to a negative OR gate by constructing a simple circuit using NOT and OR gates and verify the truth table experimentally.




3. Perform NOR operation on decimal inputs 10, 13, and 7. Convert the decimal input to the 4 bits binary form before performing the operations. Draw the timing diagram for the output in relation to the three inputs of the above gates.

Convert the decimal inputs to 4-bit binary


1. 10 (decimal) = 1010 (binary)
2. 13 (decimal) = 1101 (binary)
3. 7 (decimal) = 0111 (binary)

Bit Position	Input A (10)	Input B (13)	Input C (7)	OR Operation	NOR Operation (Output)
Bit 3 (MSB)	1	1	0	$1 \text{ OR } 1 \text{ OR } 0 = 1$	0
Bit 2	0	1	1	$0 \text{ OR } 1 \text{ OR } 1 = 1$	0
Bit 1	1	0	1	$1 \text{ OR } 0 \text{ OR } 1 = 1$	0
Bit 0 (LSB)	0	1	1	$0 \text{ OR } 1 \text{ OR } 1 = 1$	0


Input A (Decimal 10: 1010):

 

Input B (Decimal 13: 1101):

 

Input C (Decimal 7: 0111):

 

Output (NOR Result: 0000):




4. Perform NAND operation on decimal inputs 6, 9, and 11. Convert the decimal input to the 4 bits binary form before performing the operations. Draw the timing diagram for the output in relation to the three inputs of the above gates.

Convert the decimal inputs to 4-bit binary


1. 6 (decimal) = 0110 (binary)
2. 9 (decimal) = 1001 (binary)
3. 11 (decimal) = 1011 (binary)

Time (Bit)	A (6)	B (9)	C (11)	A+B+C	NAND
Bit 3	0	1	1	0	1
Bit 2	1	0	0	0	1
Bit 1	1	0	1	0	1
Bit 0	0	1	1	0	1

Timing Diagram

 

Circuit Diagram

 

5. Based on the input and output sequences given below, identify the corresponding logic operation performed on the inputs. Draw the timing diagrams of the output in relation to the inputs.

a. Input sequence A: 1 0 0 1



Input sequence B: 1 1 0 1

Input sequence C: 0 1 1 1

Output sequence: 1 1 1 0

A	B	C	Output	AND	NAND
1	1	0	1	0	1
0	1	1	1	0	1
0	0	1	1	0	1
1	1	1	0	1	0

∴ 3 input NAND gate

  

b. Input sequence A: 0 1 0 1

Input sequence B: 0 1 1 0

Output sequence: 0 0 1 1

